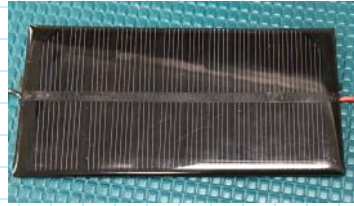


# Energy harvesting board testing 1029


2019年10月29日 星期二 15:15

1. Apparatus :

Solar cell 1 :




Solar cell 2 :

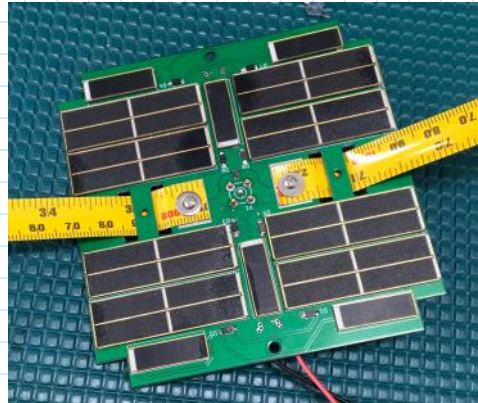


Battery :




Energy Harvesting Board:

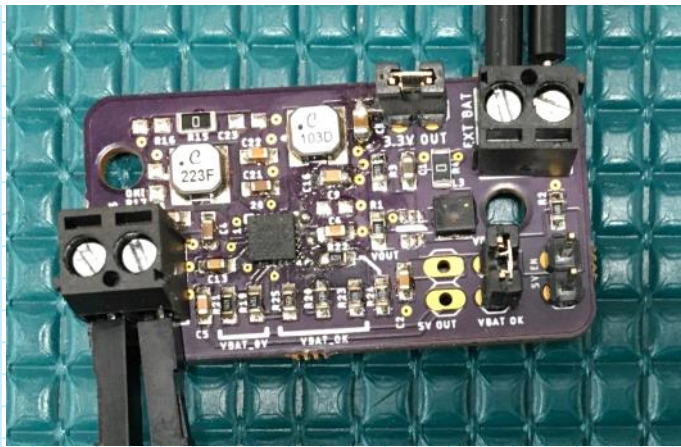


Potentiometer.

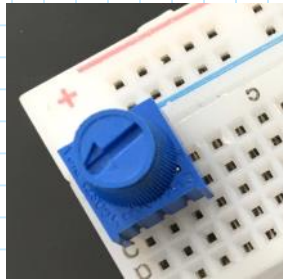

2. Test 2 PCB parallel with potentiometer.

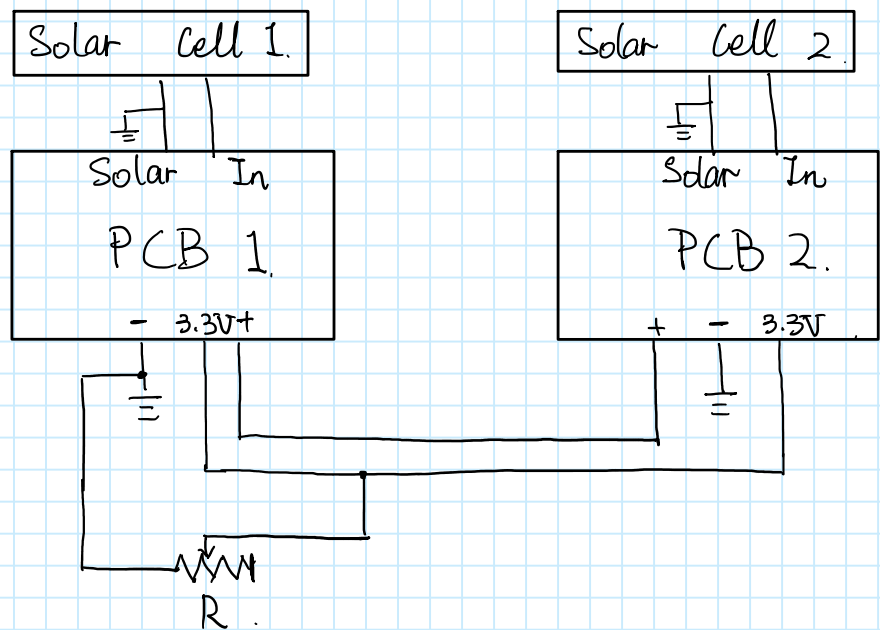

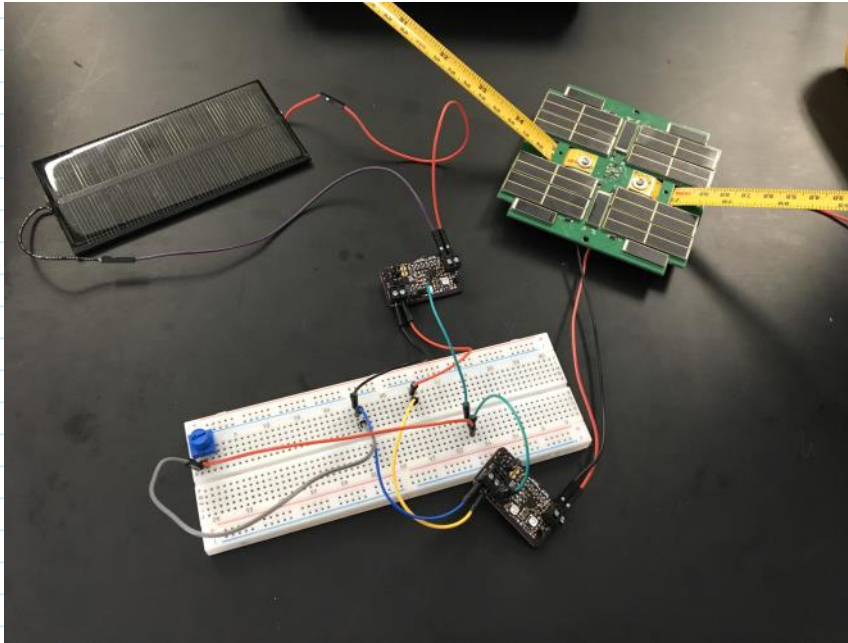

Case 1:  $R = 100 [\Omega]$ .

Solar cell 1: 1.2 [V].

Solar cell 2: 1.0 [V].

PCB 1: EXT BAT: jumping 2.3 - 3.0 [V].

3.3V OUT: jumping 0 - 0,12 [V].

PCB 2: EXT BAT: jumping 2.3 - 3.0 [V].

3.3V OUT: jumping 0 - 0,12 [V].

Case 2:  $R = 56,3 [\Omega]$ .

Solar cell 1: 1.2 [V].

Solar cell 2: 1.0 [V].

PCB 1: EXT BAT: jumping 2.3 - 3.0 [V].

3.3V OUT: jumping 0 - 0,05 [V].

PCB 2: EXT BAT: jumping 2.3 - 3.0 [V].

3.3V OUT: jumping 0 - 0,05 [V].

Case 3:  $R = 216 [\Omega]$ .

Solar cell 1: 1.2 [V].

Solar cell 2: 1.0 [V].

PCB 1: EXT BAT: jumping 2.3 - 3.0 [V].

3.3V OUT: jumping 0 - 0,2 [V].

PCB 2: EXT BAT: jumping 2.3 - 3.0 [V].

PCB 2:      2.2V OUT:    jumping    0 - 0,2 [V].  
              EXT BAT:    jumping    2.3 - 3.0 [V]  
              3.3V OUT:    jumping    0 - 0,2 [V].

All cases indicate that current through 3.3V OUT is around 1 [mA].